

CIRCUIT DIAGRAM OF FULL ADDER

EXPERIMENT No: 7

TITLE: Design of Full Adder using VHDL Code


OBJECTIVE: To design a full adder using VHDL code

Software used: Xilinx ISE Project Navigator

Software tools used: ISE 14.7 Simulator

THEORY: A Full adder is a Combinational circuit that performed the arithmetic sum of 3 inputs bits. It consist of 3 inputs & 2 output. Those of the input variables can be defined as A, B, C i.e. & the two output variables can be defined earlier Cout & B. The two input variable that are defined earlier A & B represent the carry bit. The 2 input significant bits to be added. The 3rd input C_{in} represent the carry bit. We have to use two digit because the arithmetic sum of the 3 binary digits needs two digits. The two output represent for sum & cost for carry.


7 of 10

 

Truth Table of Full Adder

	INPUT			OUTPUT	
	A	B	Cin	S	Count
	0	0	0	0	0
	0	0	1	1	0
	0	1	0	1	0
	0	1	1	0	1
	1	0	0	1	0
	1	0	1	0	1
	1	1	0	0	1
	1	1	1	1	1

FULL ADDER

 

Teacher's Signature

VHDL Code for FULL ADDER

Library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity FULL_ADDER is

Port (A: in STD_LOGIC;

B: in STD_LOGIC;

Cin: in STD_LOGIC;

S: out STD_LOGIC;

Cout: out STD_LOGIC);

end FULL_ADDER;

architecture Behavioral of FULL_ADDER is

begin

S <= A XOR B XOR Cin;

Cout <= ((A AND B) OR (B AND Cin) OR (A AND Cin));

end Behavioral;

Teacher's Signature

VHDL TEST BENCH Code for FULL ADDER :-

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY FULLADDER_TESTBENCH IS

END FULLADDER_TESTBENCH;

ARCHITECTURE behavior OF FULLADDER_TESTBENCH IS

COMPONENT FULL_ADDER

PORT (

A: IN std_logic;

B: IN std_logic;

Cin: IN std_logic;

S: OUT std_logic;

Cout: OUT std_logic;

);

END COMPONENT;

Signal A: std_logic := '0';

Signal B: std_logic := '0';

Signal Cin: std_logic := '0';

Signal S: std_logic;

Signal Cout: std_logic;

BEGIN

unt: FULLADDER PORT MAP (

A => A1

B => B1

Cin => Cin

S => S1

Cout => Cout

);

stim - proc : process

begin

A <= '0';

B <= '0';

Cin <= '0';

wait for 20 ns;

A <= '0';

B <= '0';

Cin <= '1';

wait for 20 ns;

A <= '0';

B <= '1';

Cin <= '0';

wait for 20 ns;

A <= '0';

B <= '1';

Cin <= '1';

Teacher's Signature

```
wait for 20 ns;
```

```
A <= '1';
```

```
B <= '0';
```

```
Cin <= '0';
```

```
wait for 20 ns;
```

```
A <= '1';
```

```
B <= '0';
```

```
Cin <= '1';
```

```
wait for 20 ns;
```

```
A <= '1';
```

```
B <= '1';
```

```
Cin <= '0';
```

```
wait for 20 ns;
```

```
A <= '1';
```

```
B <= '1';
```

```
Cin <= '1';
```

```
wait for 20 ns;
```

```
end process;
```

```
END;
```

CONCLUSION: In this experiment we were introduced with the produce of designing a full adder using VHDL. It is a Combinational circuit we have to use the logic in VHDL in this experiment. We also have written the corresponding VHDL Testbench & successfully verified the simulation result with the help of truth table.

Dalvi
23/3

Teacher's Signature